

Convert the given Moore machine into Mealy machine
 Draw state transition diagram of Mealy machine

Present state	Next state		output
	0	1	
$\rightarrow P_0$	γ	q_0	0
P_1	γ	q_0	1
q_0	P_1	S_0	0
q_1	P_1	S_0	1
γ	q_1	P_1	0
S_0	S_1	γ	0
S_1	S_1	γ	1

Mealy machine

